

# Stability Analysis of Switched DC-DC Boost Converters for Integrated Circuits


Kevin Fronczak

Advisor: Dr. Robert Bowman

# Overview
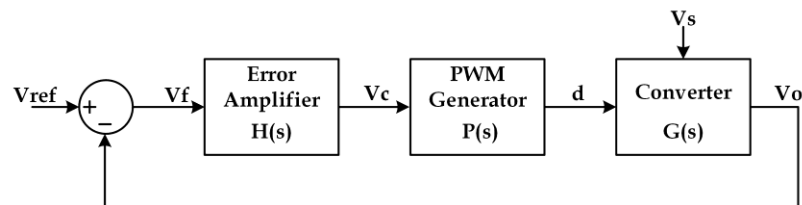
## Switched DC-DC Converters

- Why does stability matter?
- How does the architecture affect instability?
- How does component variability affect stability?
- What methods are used to minimize instability?
- How can stability be measured?




**Switched Converter Block Diagram**

# Importance of Stability
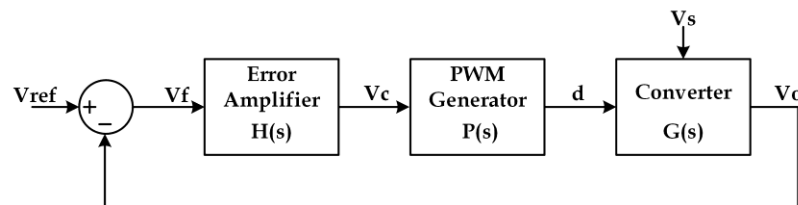
## Switched DC-DC Converters


- Supply oscillations can couple into signal paths
  - Sensitive circuits suffer
- Unstable supply = inaccurate supply
- Inaccurate supply = performance degradation



**Switched Converter Block Diagram**

# Importance of Stability

## Display Driver Block Diagram

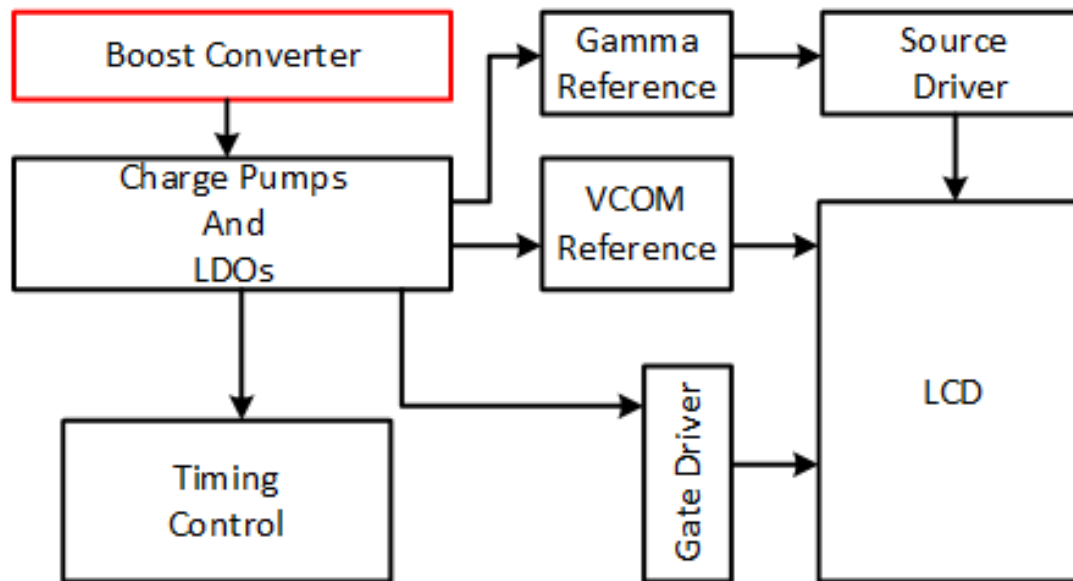


Adapted from Yang-Ching Lin *et. al.* (2012)

# Importance of Stability
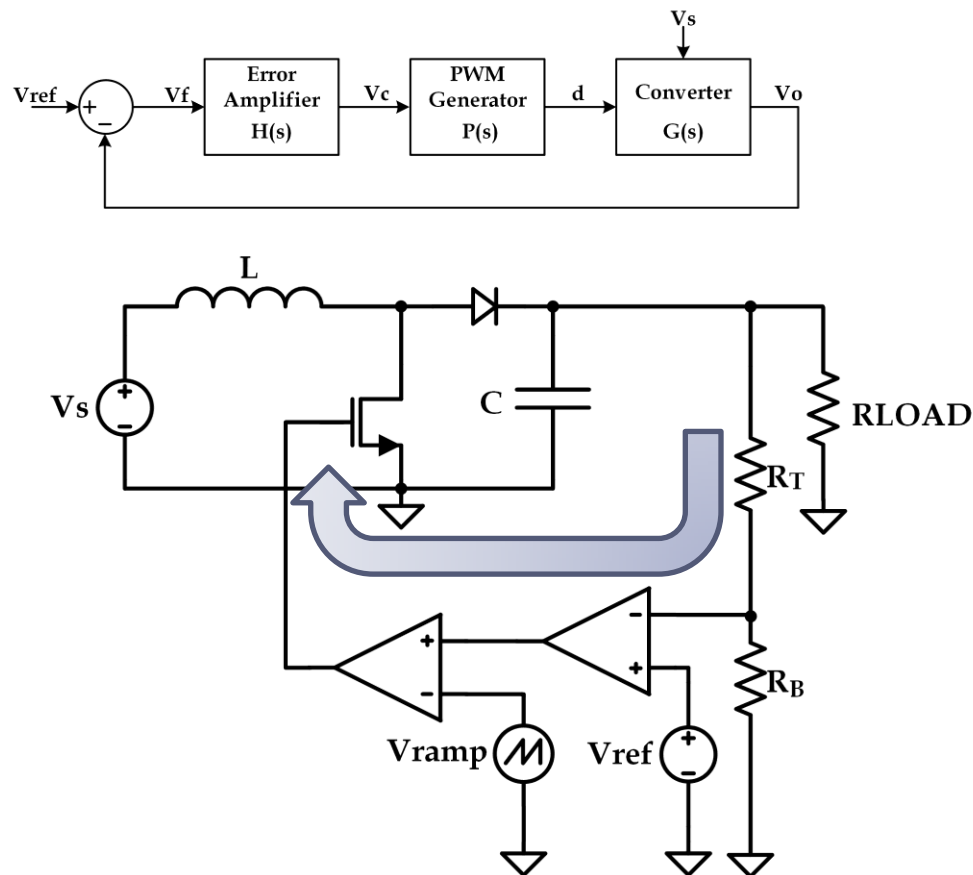
## Boost Converter Architecture



- Feedback loop
  - Chance of oscillation at output



# Causes of Instability
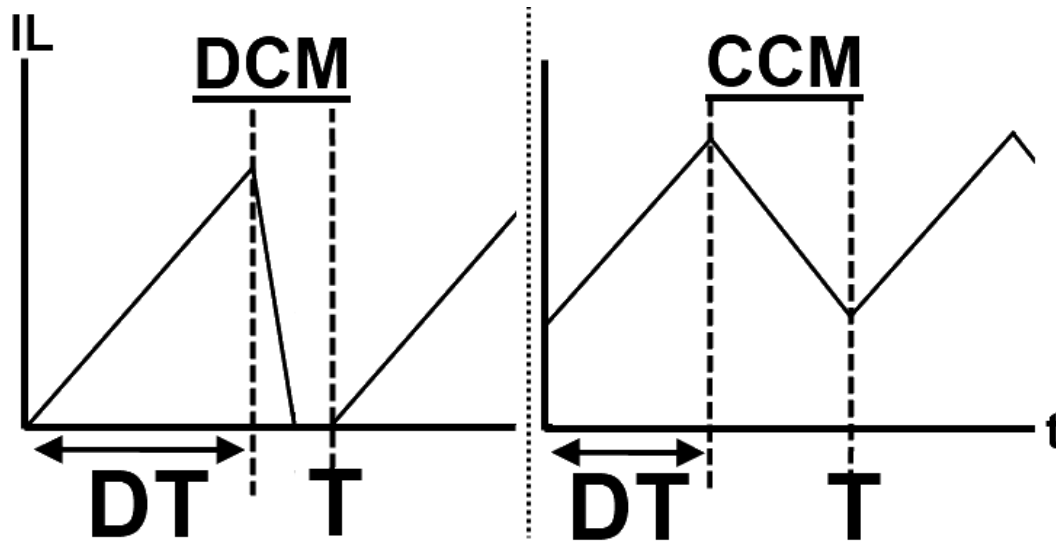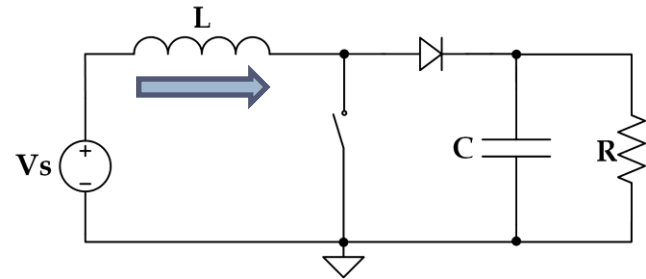
## Operating Modes

- Operating Mode
  - CCM (Continuous Conduction Mode)
  - DCM (Discontinuous Conduction Mode)




# Causes of Instability


## Small-Signal Modeling

### Average PWM Switch


Vorperian (1990)

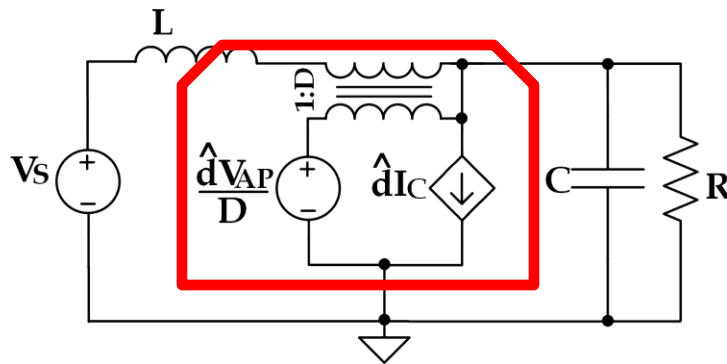

**Continuous Mode**

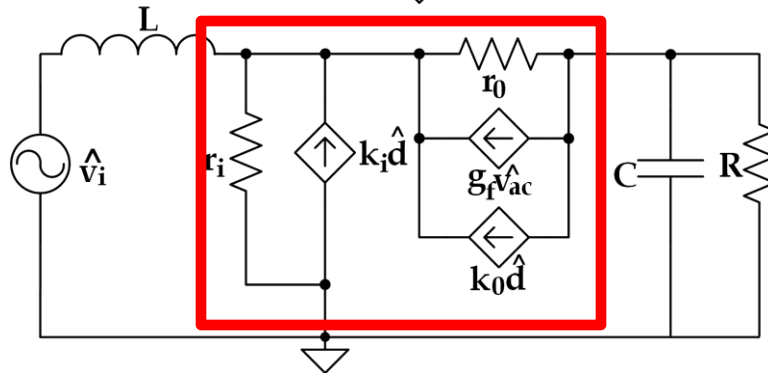



**Discontinuous Mode**

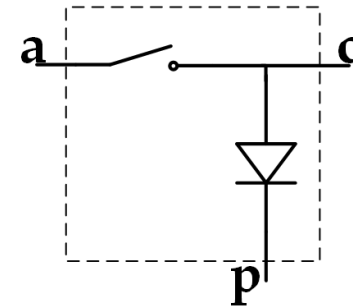

# Causes of Instability (CCM)
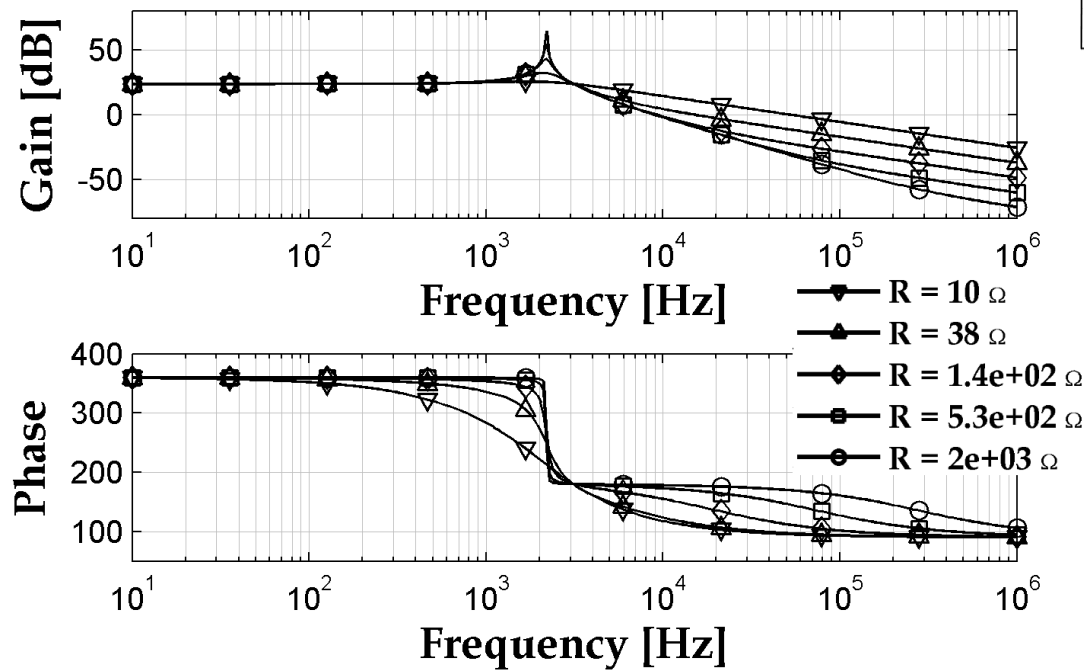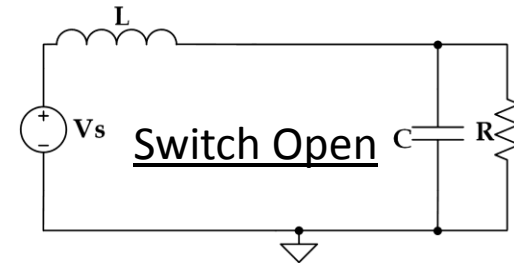
## Bode Plot for Continuous Mode

- CCM has conjugate pole
  - LC Resonance




$$\omega_0 = \frac{1 - D}{\sqrt{LC}}$$

$$Q = R(1 - D)\sqrt{\frac{C}{L}}$$



# Causes of Instability (CCM)


Input Step Response for Continuous Mode

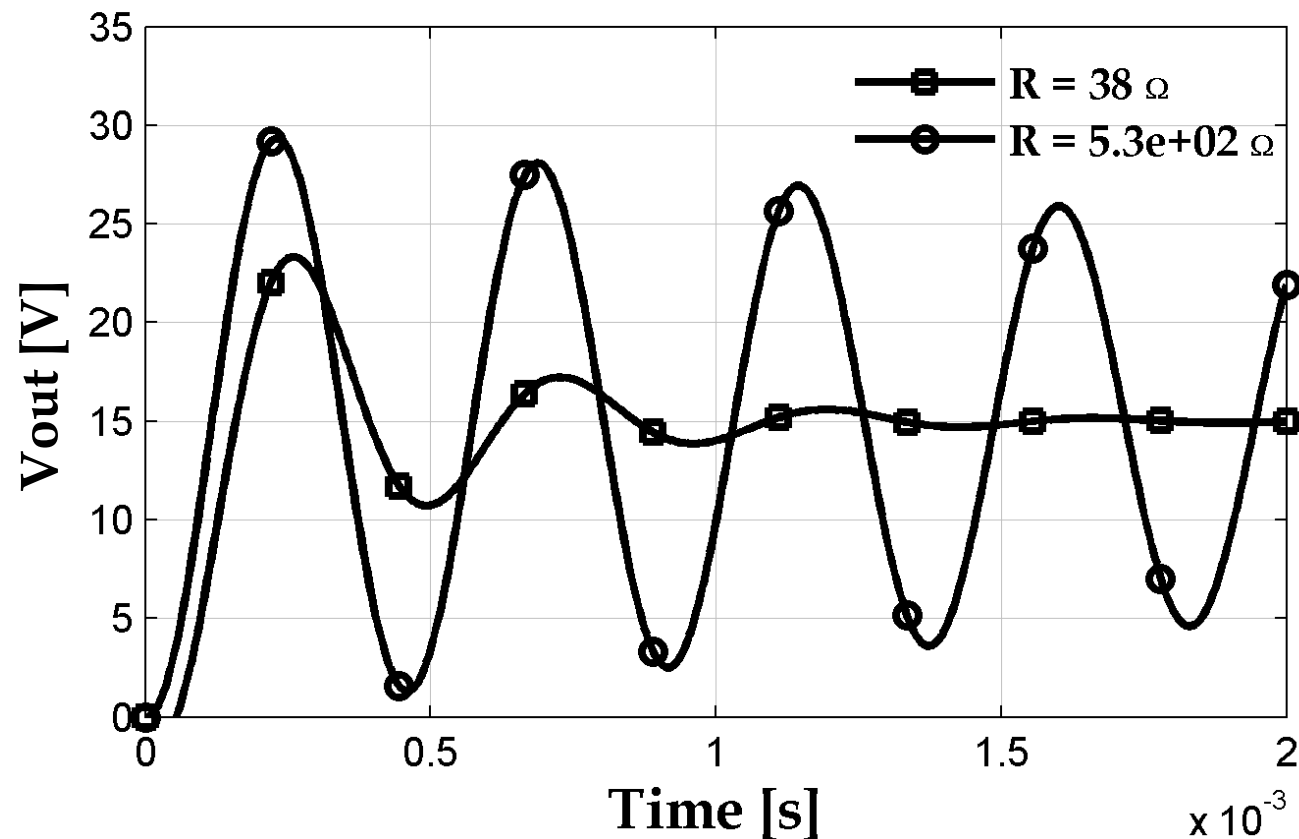

# Causes of Instability (DCM)

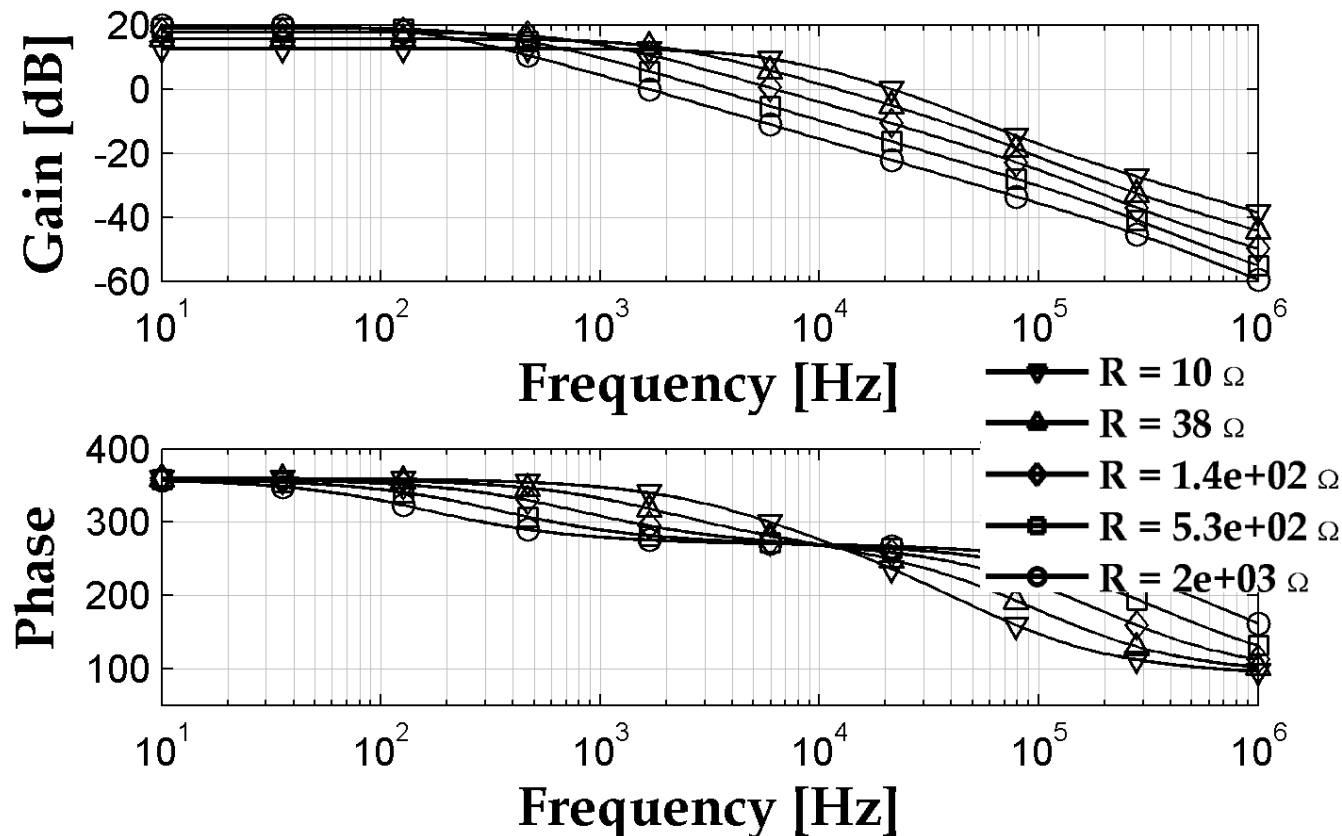
## Bode Plot for Discontinuous Mode

- DCM Appears 1<sup>st</sup> order at low frequencies



# Causes of Instability (DCM)


## Change in Gain for Discontinuous Mode

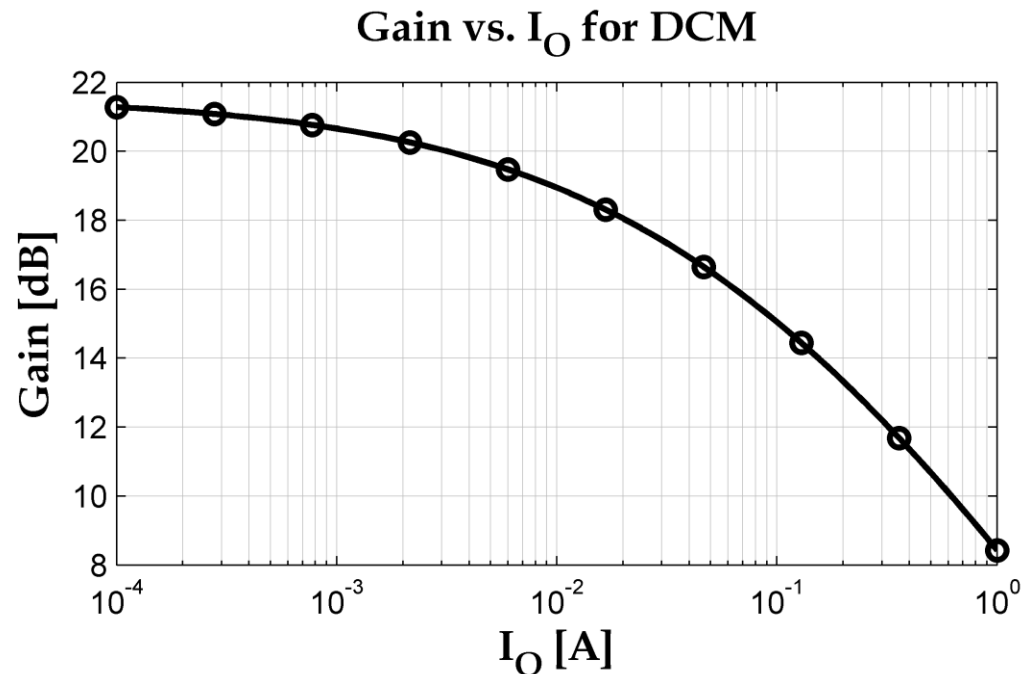

$$G_{d0} = \frac{2V_O}{\sqrt{\frac{LF_S I_O}{2V_O} \left[ \left( 2\frac{V_O}{V_S} - 1 \right)^2 - 1 \right]} + 1}$$

# Causes of Instability (DCM)

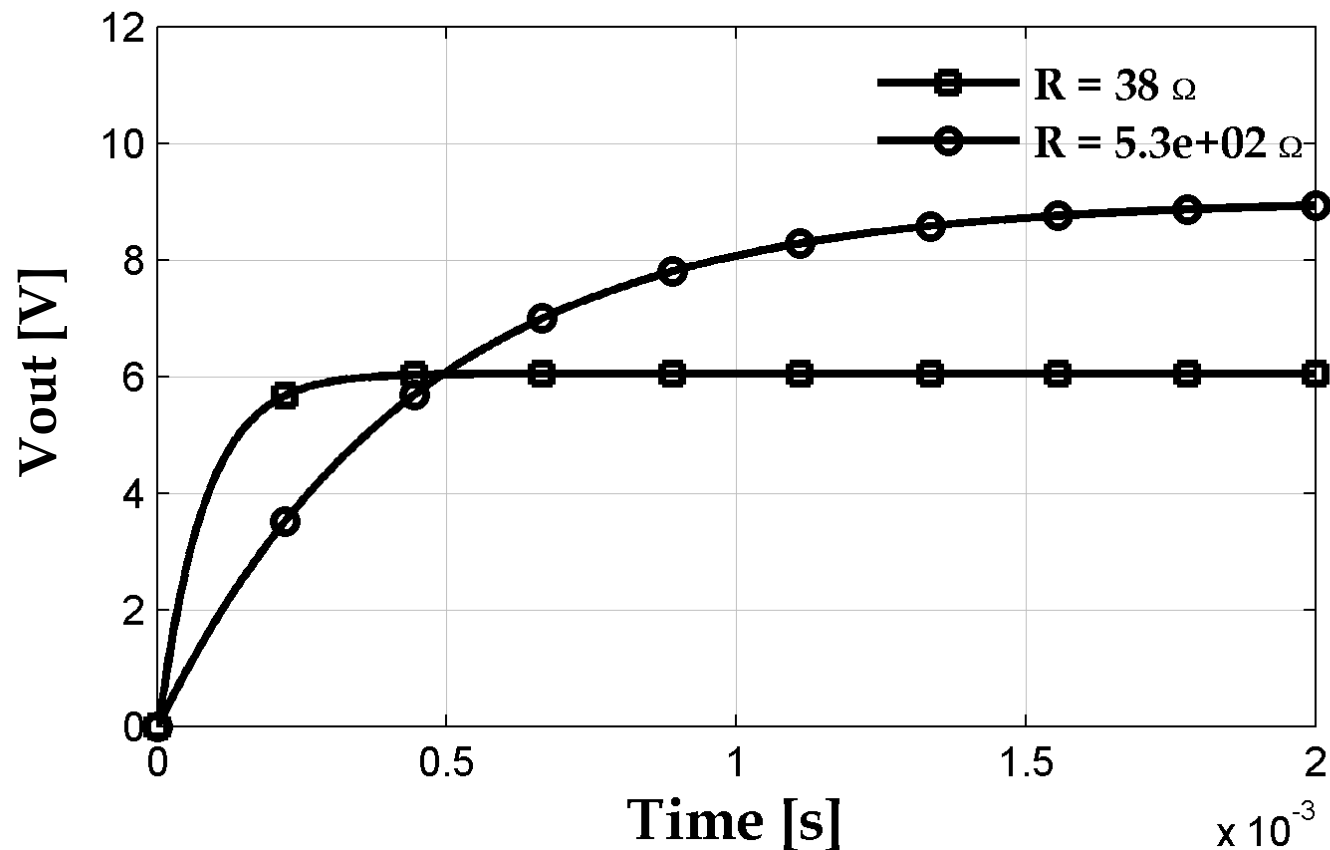
## Input Step Response for Discontinuous Mode



# Parasitic Component Effects
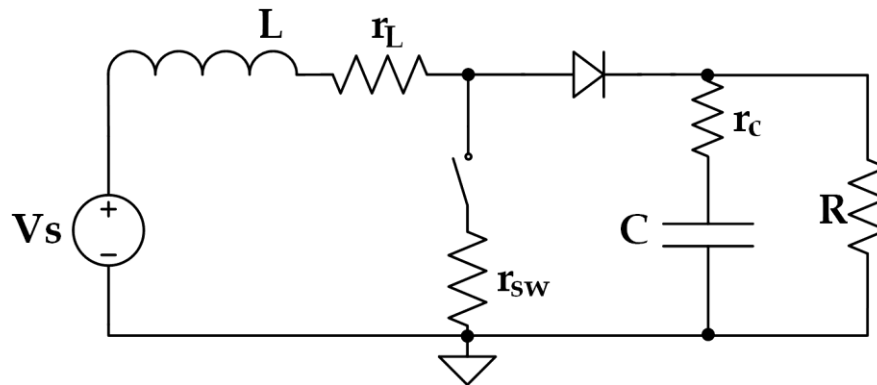
## Non-ideal Converter Schematic

- Inductor has series resistance
  - Lowers height of resonant peak (CCM)
- Capacitor has series resistance
  - Adds high-frequency zero
  - Less attenuation at frequencies  $> F_s$





# Parasitic Component Effects
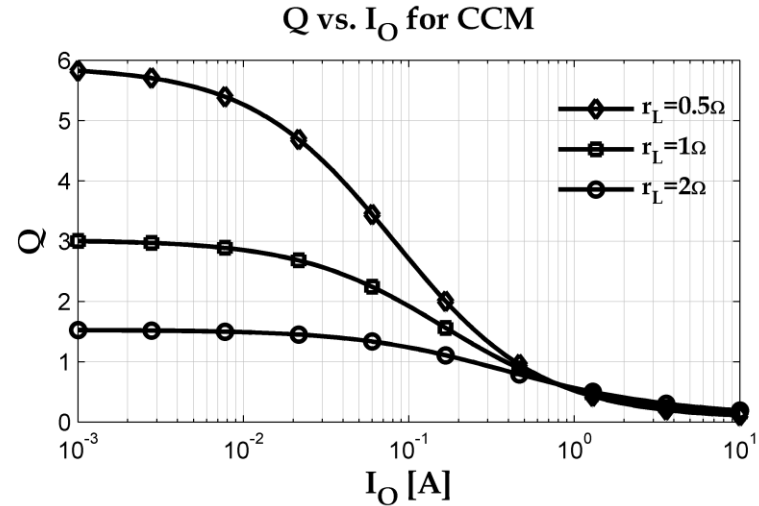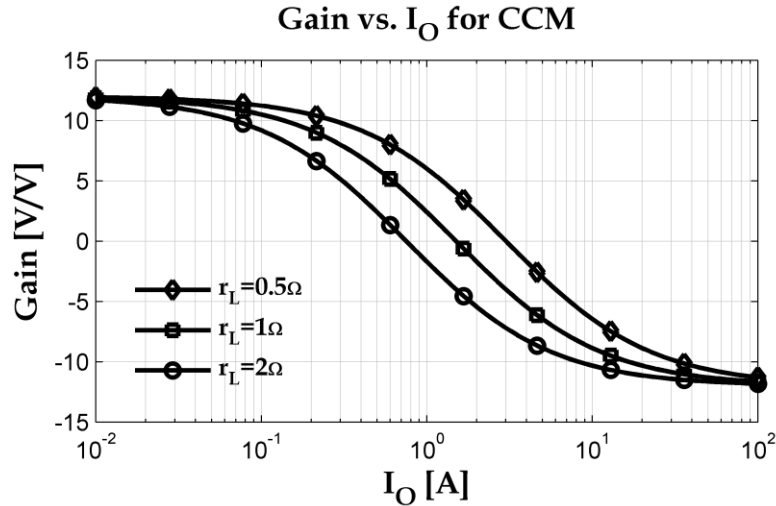
## Continuous Mode: Expected Behavior

$$G_{d0} = \frac{V_O}{1-D} \frac{R(1-D)^2 - r_L}{R(1-D)^2 + r_L}$$


$$Q = \sqrt{LC} \frac{\sqrt{(R+r_C)(R(1-D)^2 + r_L)}}{Rr_C C(1-D)^2 + Rr_L C + r_C r_L C + L}$$



# Parasitic Effects (CCM)

## Bode Plot for Continuous Mode


- Bode Plot

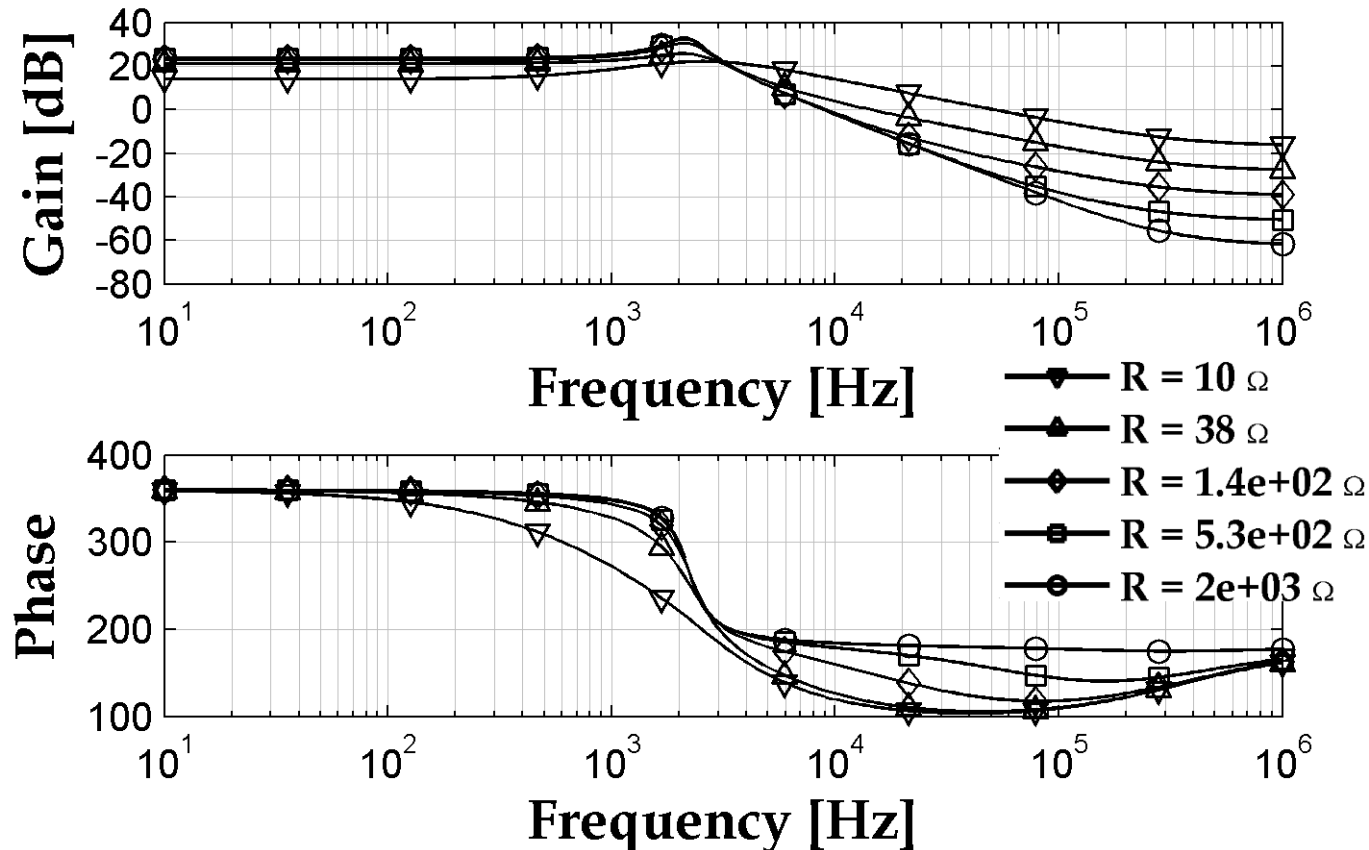

# Parasitic Effects (DCM)

## Bode Plot for Discontinuous Mode

- Bode Plot

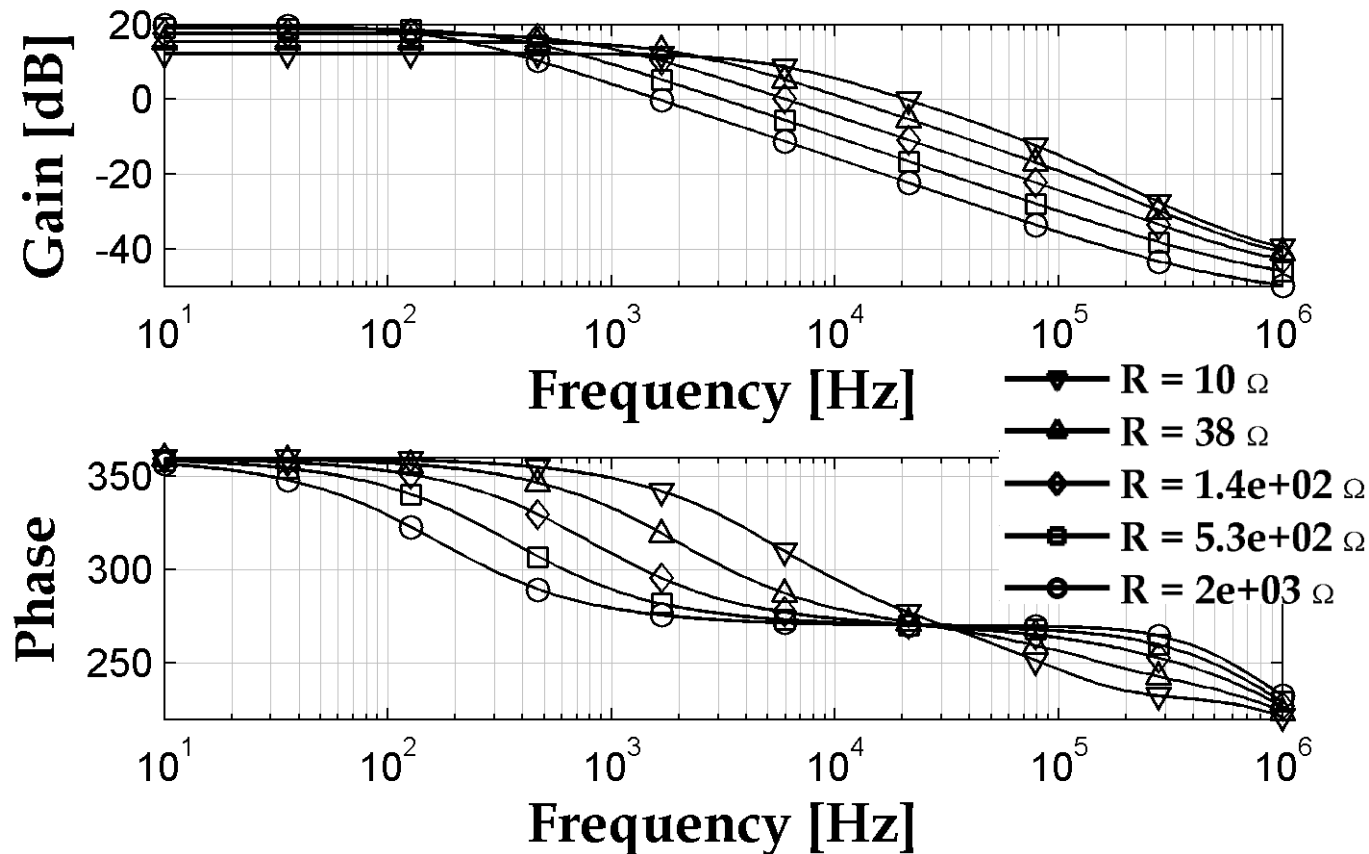




# Component Variation


## Effect on Phase Margin

- Input Voltage, Load Current, Inductance
  - $V_o/V_s = [3.3, 2, 1.4]$
  - $I_o = [6 \text{ mA}, 30 \text{ mA}, 54 \text{ mA}]$  (DCM);  $[150 \text{ mA}, 300 \text{ mA}, 450 \text{ mA}]$  (CCM)
  - $L = [15 \text{ } \mu\text{H}, 20 \text{ } \mu\text{H}, 25 \text{ } \mu\text{H}]$  (DCM);  $[170 \text{ } \mu\text{H}, 200 \text{ } \mu\text{H}, 230 \text{ } \mu\text{H}]$  (CCM)

Phase Margin for Corners of DCM Boost

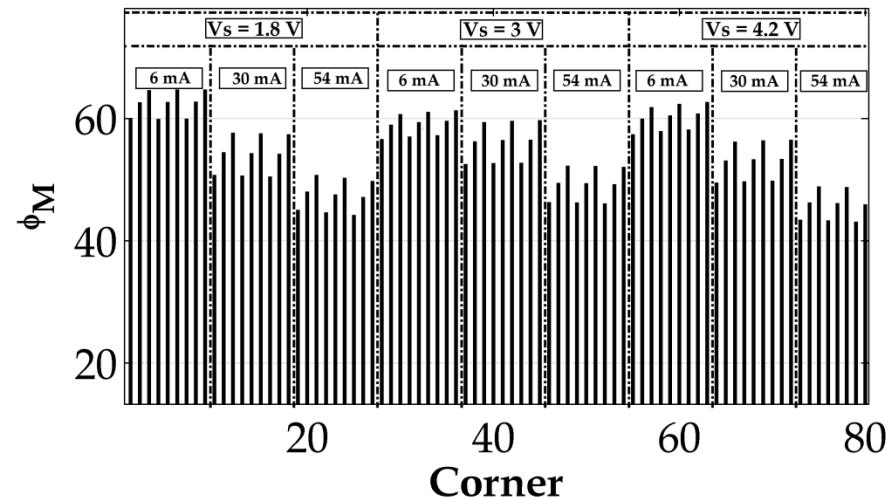

Phase Margin for Corners of CCM Boost

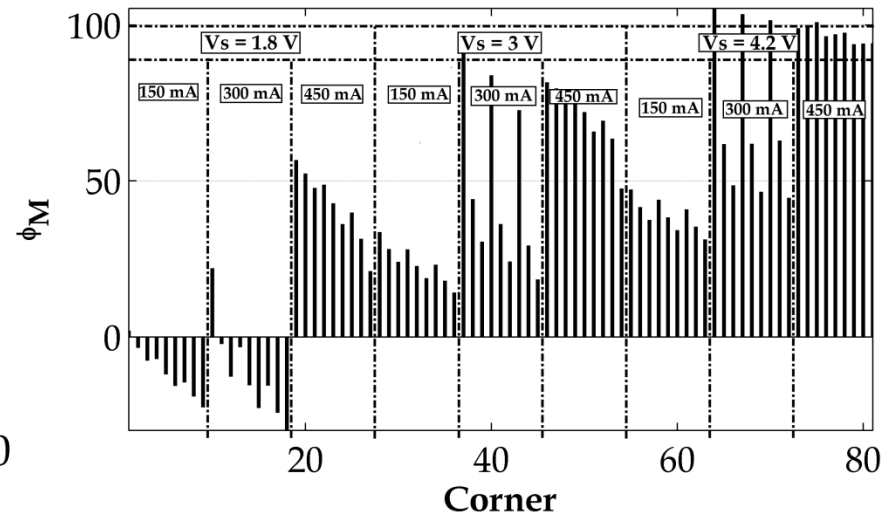


\*Note – all values calculated for converter WITH control

# Component Variation


## Effect on DC-Gain

- Input Voltage, Load Current, Inductance
  - $V_o/V_s = [3.3, 2, 1.4]$
  - $I_o = [6 \text{ mA}, 30 \text{ mA}, 54 \text{ mA}]$  (DCM);  $[150 \text{ mA}, 300 \text{ mA}, 450 \text{ mA}]$  (CCM)
  - $L = [15 \text{ } \mu\text{H}, 20 \text{ } \mu\text{H}, 25 \text{ } \mu\text{H}]$  (DCM);  $[170 \text{ } \mu\text{H}, 200 \text{ } \mu\text{H}, 230 \text{ } \mu\text{H}]$  (CCM)

DC Gain for Corners of DCM Boost

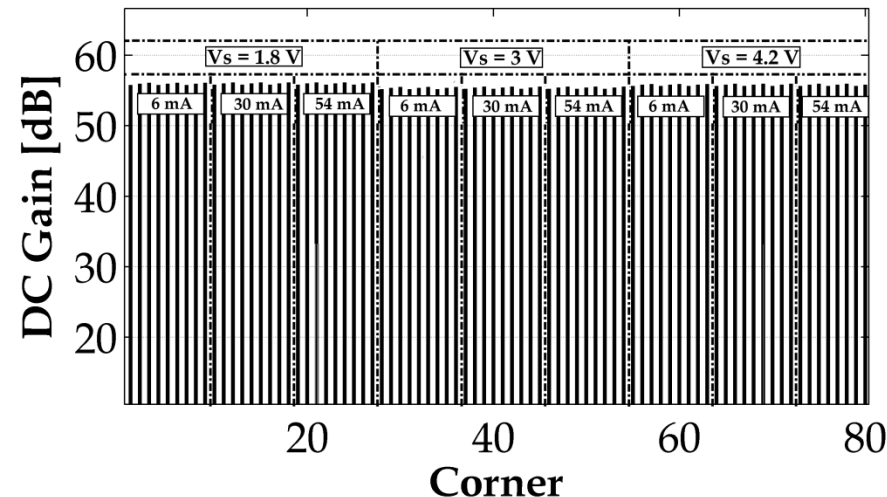

DC Gain for Corners of CCM Boost

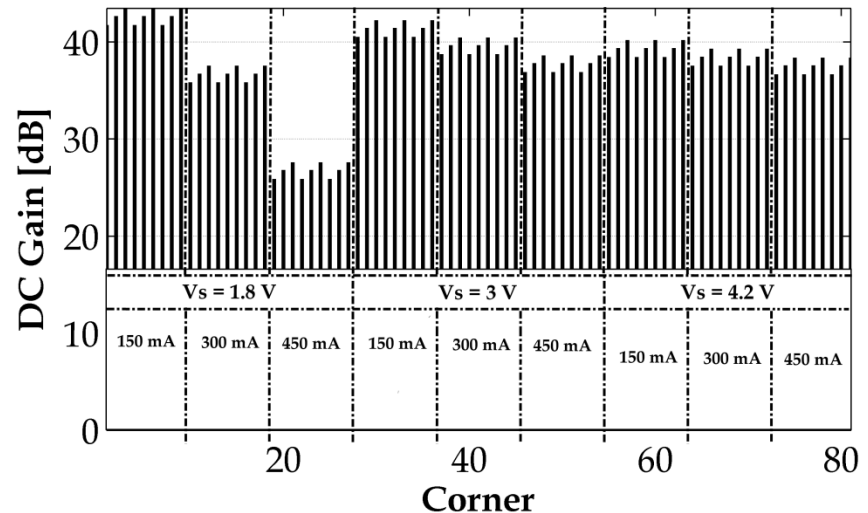

\*Note – all values calculated for converter WITH control

# Control of Converters



## Error Amplifier Requirements

- Control needs to help provide stable output
  - Requires feedback loop → source of instability
  - Needs to minimize output error (large gain)
  - Needs to minimize instability (large phase margin)
  - Needs to maximize speed (large bandwidth)
- Op Amps/OTAs
  - Op Amps
    - Voltage buffer → Slows down performance
    - Can drive low impedances
  - OTAs
    - Can't drive resistive loads
    - Fast → does not have voltage buffer (response limited by load capacitance)

# Control of Converters (CCM)
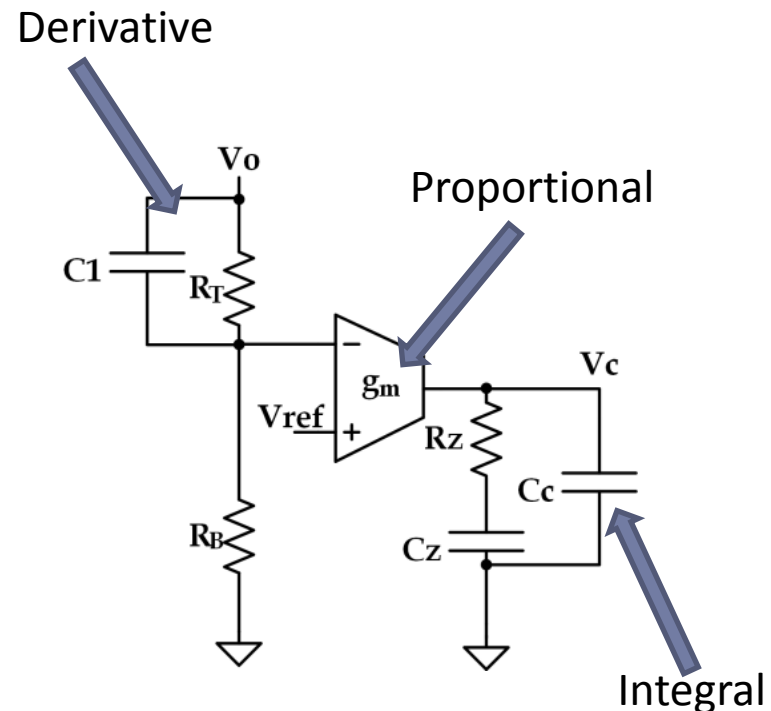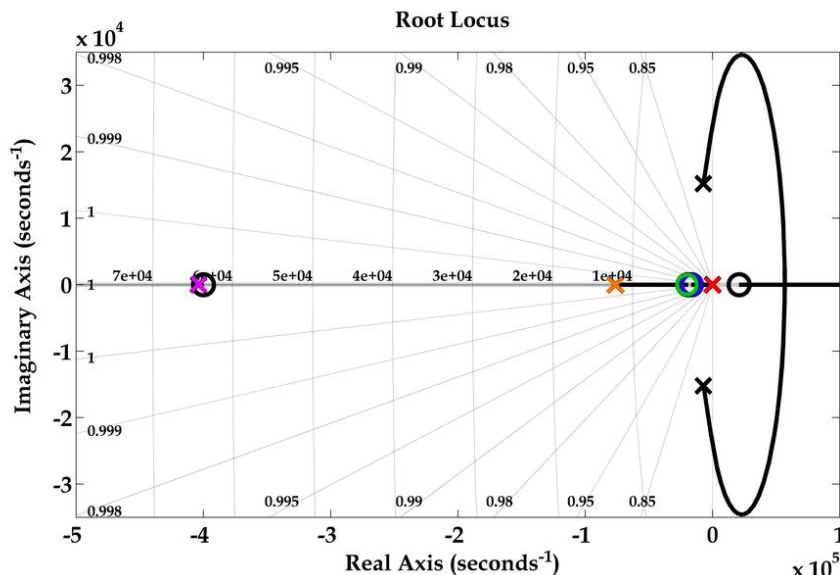
## Proportional-Integral-Derivative Architecture

- PID Required for CCM
  - Two poles, two zeros
    - Minimizes conjugate pair effect





$$\frac{V_c}{V_o} = \frac{g_m R_B}{s(R_B + R_T)(C_Z + C_C) \left( s \frac{R_Z C_Z C_C}{C_Z + C_C} + 1 \right) (s(R_T \parallel R_B)C_1 + 1)}$$

# Control of Converters (CCM)
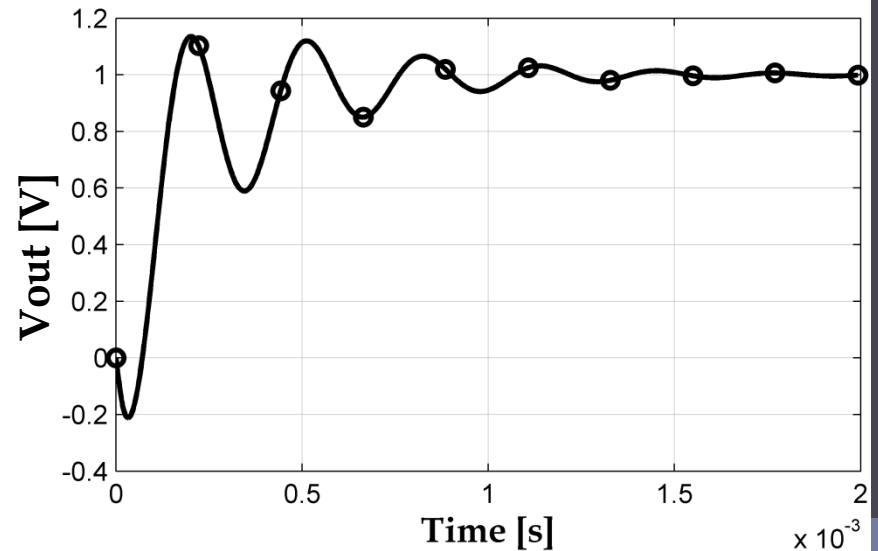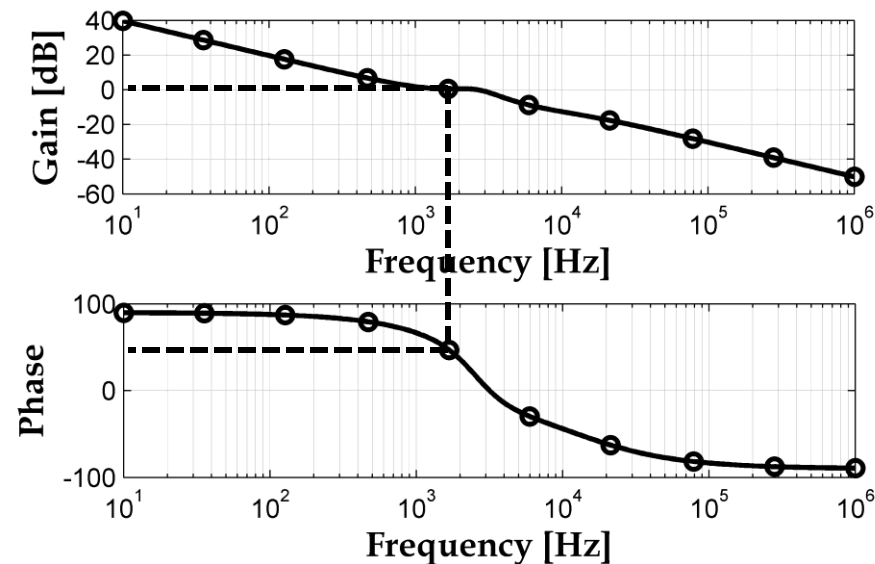
## Bode Plot and Step Response



- Difficult to achieve all three requirements
  - Gain, Phase Margin, Bandwidth



# Control of Converters (DCM)
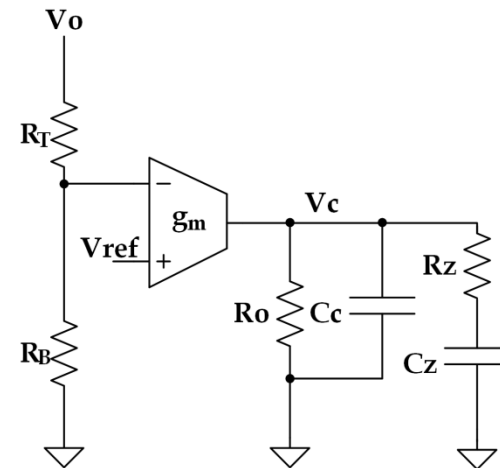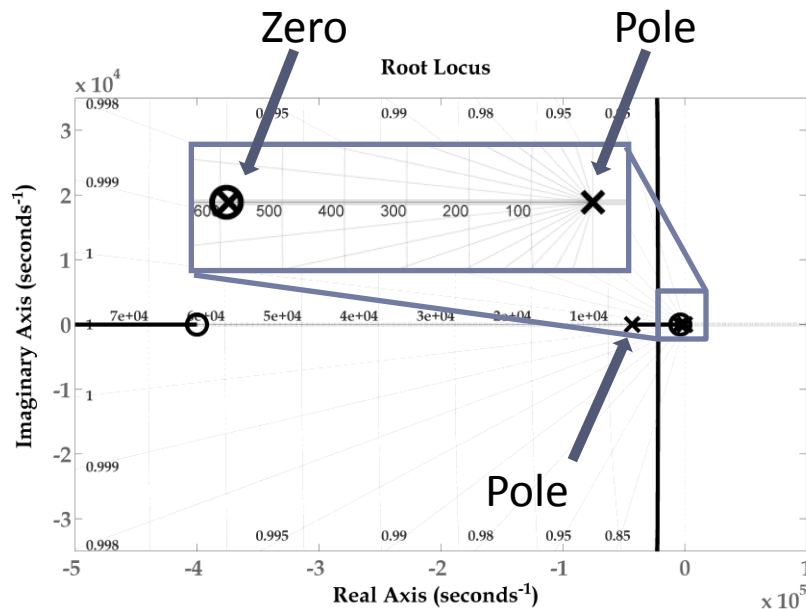
## Lag Controller Architecture

- Lag Controller suitable for DCM
  - Zero to cancel converter Pole
  - Pole to attenuate switching noise





$$\frac{V_c}{V_o} = K \frac{sR_zC_z + 1}{s^2R_oR_zC_cC_z + sR_oC_z + 1}$$

$$K = g_m R_o \frac{R_B}{R_T + R_B}$$

# Control of Converters (DCM)
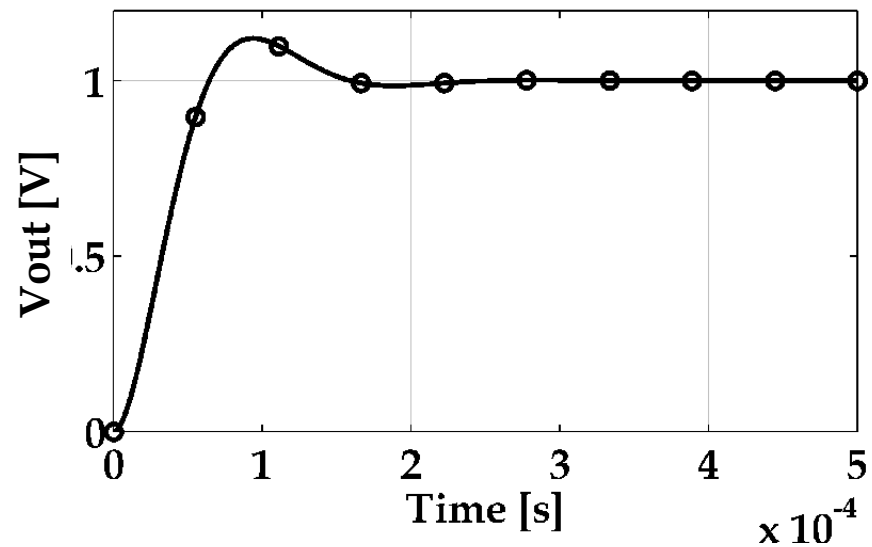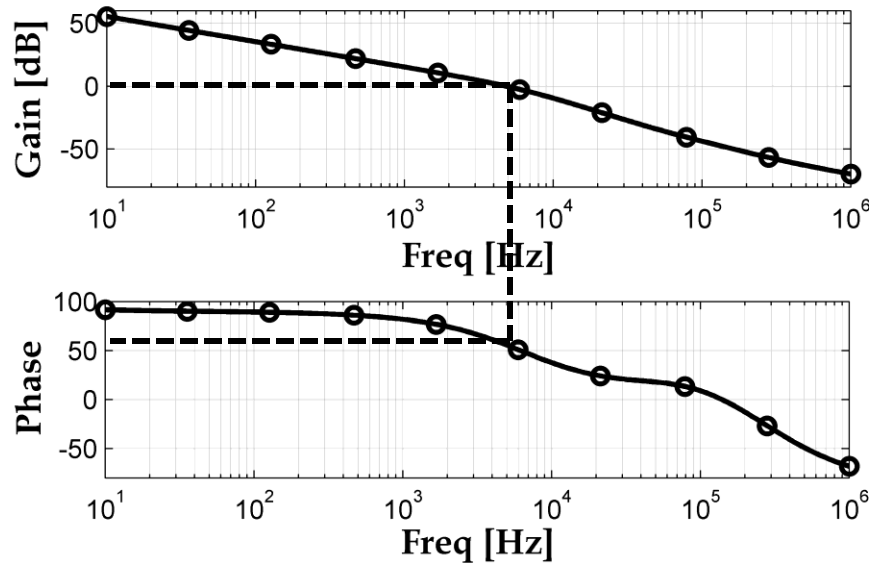
## Bode Plot and Step Response

- Easier control compared to CCM
- More stable with fewer components



# Measuring Stability

## Stability Measurement Requirements and Possibilities

- Cannot “break the loop”
  - High loop gain
- Observe step response
- Superimpose voltage (Middlebrook’s Method)
- Cross-correlation




# Measuring Stability


## Load Step Response

- Converter reaches steady state
  - Step the load current
- Composite Response of System
  - No pole/zero information

Overdamped Response

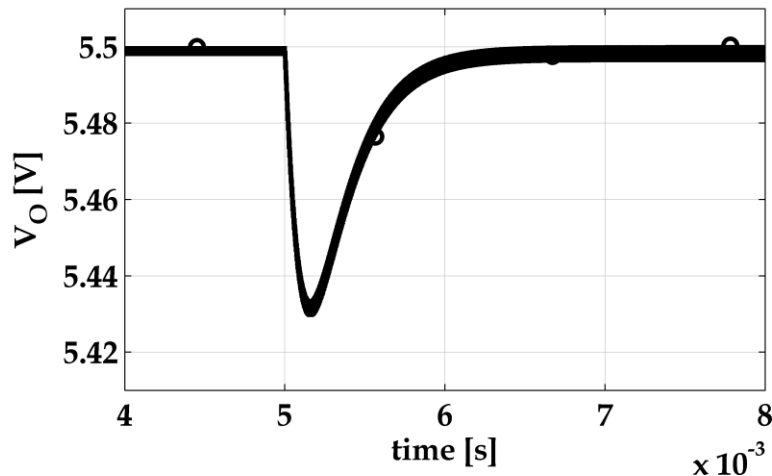


Underdamped Response

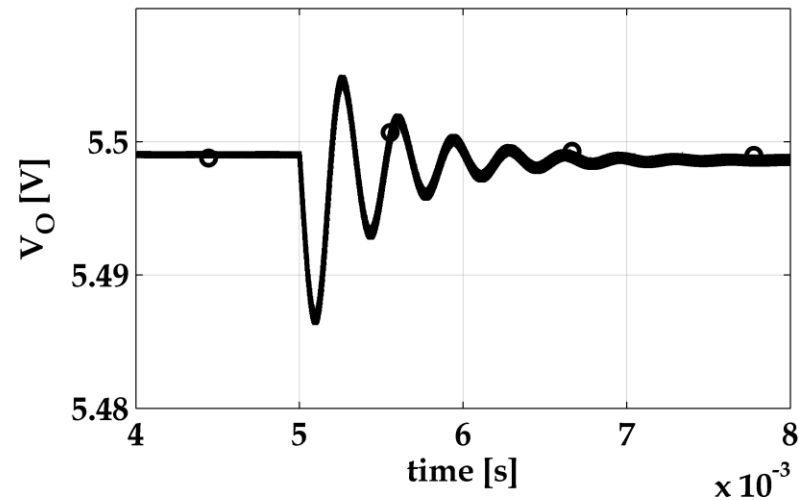


# Measuring Stability

## Middlebrook's Method (1975)

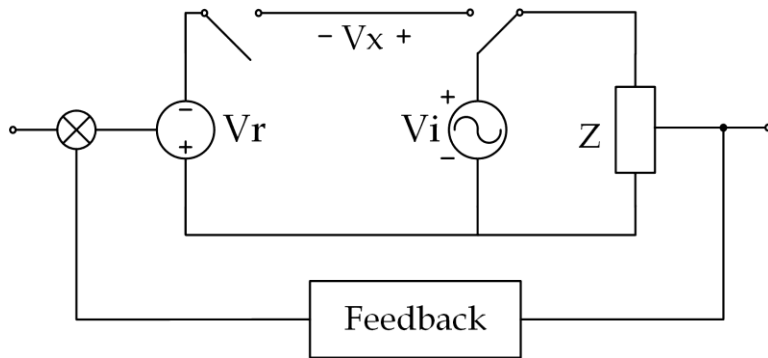

### Conventional Approach

- Voltage Injection

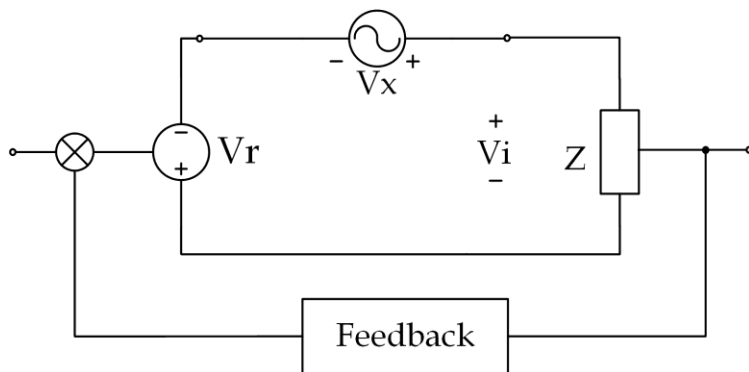


### Middlebrook's Method

- Superposition

# Measuring Stability
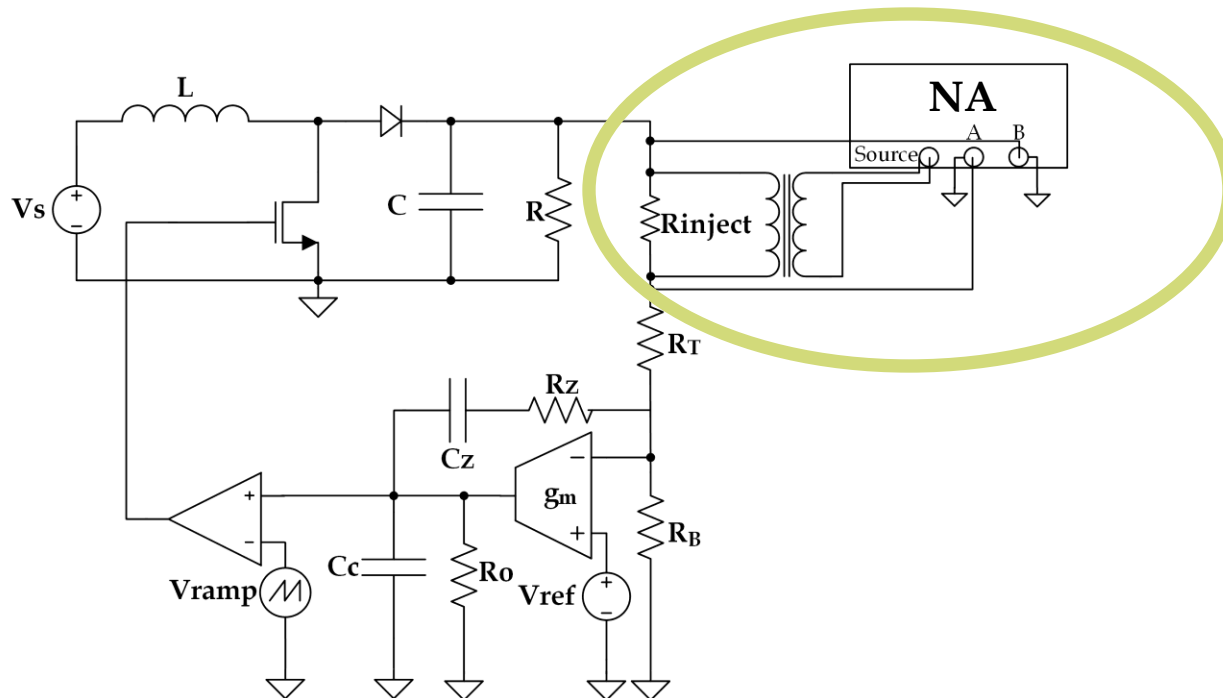
## Implementation of Middlebrook's Method

- Can measure with Network Analyzer
- Bode plot can be compared to simulations
- Gives information on overall stability
  - Pole/Zero migration can be directly observed



# Measuring Stability

## Cross Correlation with White Noise

- Inject white noise in control signal path
  - White noise has autocorrelation of delta function
    - Yields impulse response
    - FFT yield frequency response


$$(1) R_{xy}[m] = \sum_{n=-\infty}^{\infty} h[n] R_{xx}[m - n] + R_{xv}[m]$$

$$(2) R_{xx}[m] = \delta[m] \longrightarrow (3) R_{xy}[m] = h[m]$$



# Measuring Stability

## “White Noise” Circuit Implementation

## “White Noise” Circuit Implementation

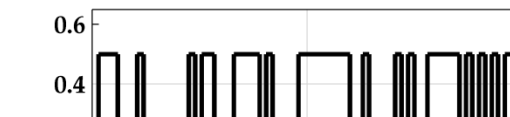- PRBS (Pseudo-Random Binary Sequence)
    - Periodic noise
      - Cross-correlation can only happen within one period
      - Period can be made larger by adding more bits to sequence
      - PRBS amplitude must be small percentage of control signal
      - Can be superimposed over  $V_{ref}$
- 


$$T_{PRBS} = \frac{2^n - 1}{f_k}$$

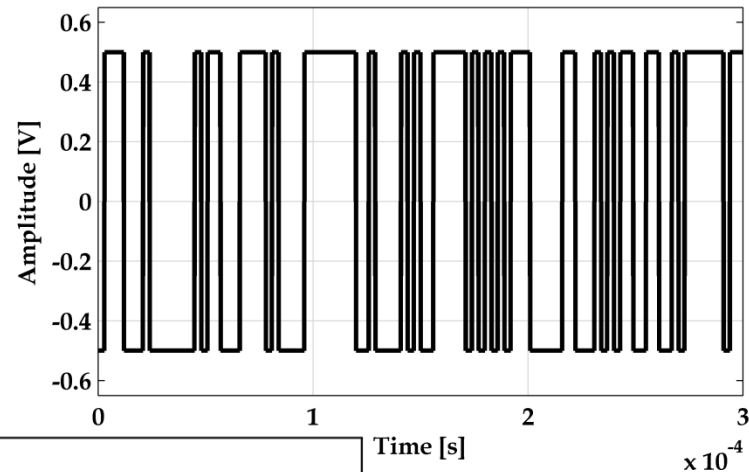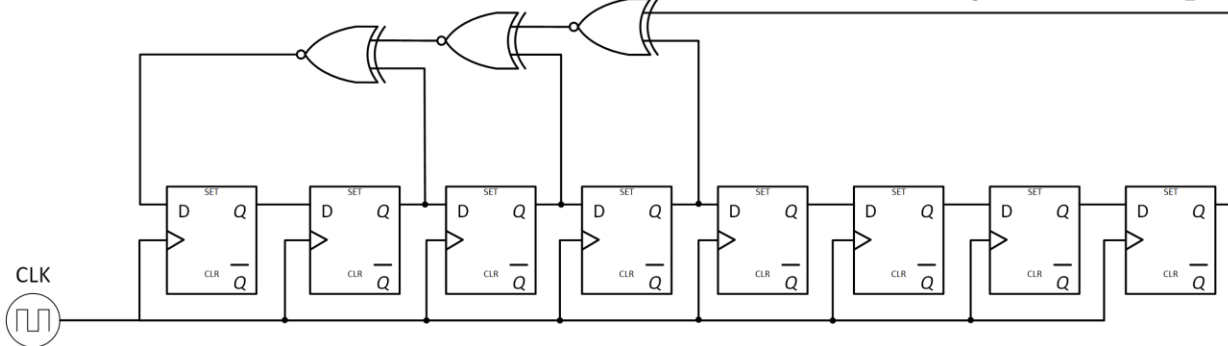


# Measuring Stability
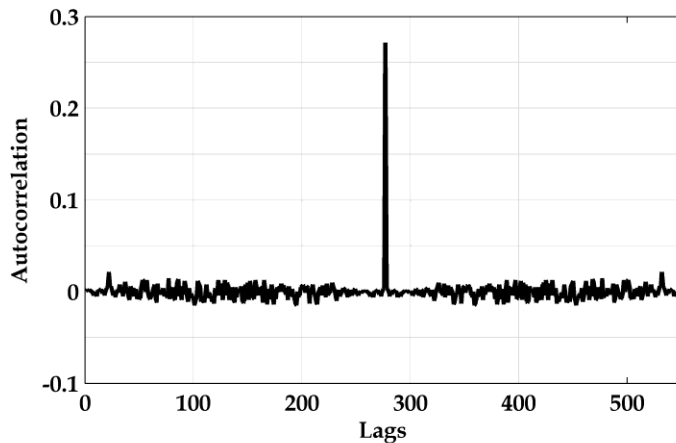
## PRBS Autocorrelation

- Single period PRBS (a) has small autocorrelation value
  - Ideally infinite
- Multi-period PRBS (b) has larger value
  - Can sample the converter response multiple times
    - Average of results gives more accurate frequency response



(a)

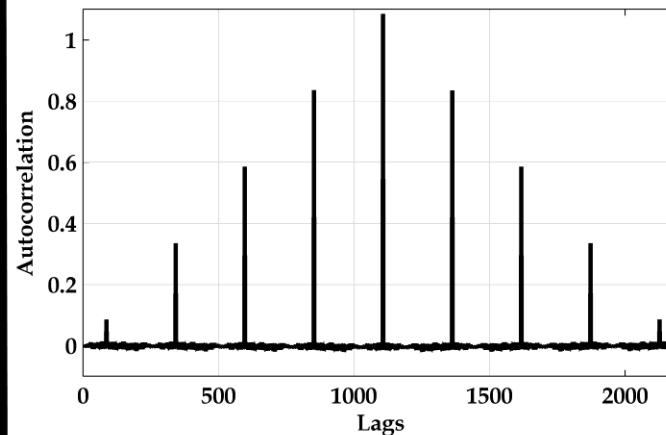

(b)

# Measuring Stability

## Frequency Response Method Comparison

- Frequency Response gives most information on circuit
  - Can directly compare bode plot to simulations
  - Can see effect of resonance (for CCM)
  - Can see effect of filter capacitor ESR zero
- Methods
  - Middlebrook's Method
    - + Simple
    - - Requires Manual Capture
  - Cross-correlation (PRBS)
    - + Allows for Built-In Self-Test (BIST)
    - - Adds complexity

# Summary

- DCM = Easier to Control
- Controller Design = Simple for DCM, Complex for CCM
- Frequency Response = Vital in determining stability
  - Two techniques: Middlebrook, Cross Correlation

## Future Work

- Controller design via optimization algorithms
  - Genetic Algorithms, Particle Swarm Optimization
- More in-depth exploration of PRBS
  - On-chip Supply Testing



# Thank You

- Comments/Questions?